



Outline

Week 5: Circuits


Course Notes: 3.5

Goals: Use linear algebra to determine voltage drops and branch currents.


Components in Resistor Networks

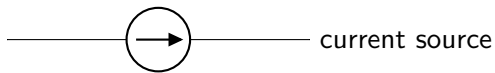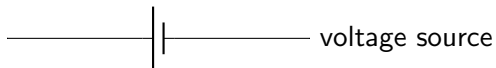



Components in Resistor Networks

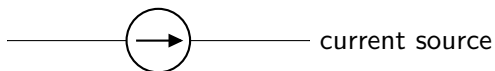


Components in Resistor Networks

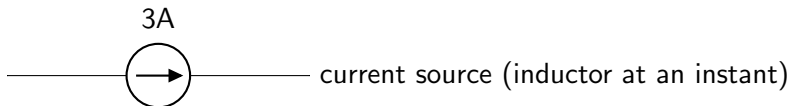


Components in Resistor Networks

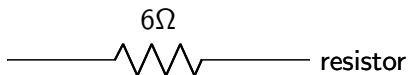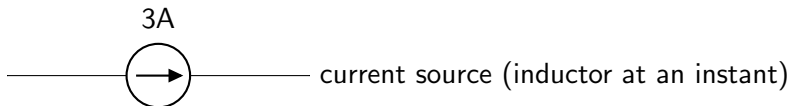


$$V = IR$$

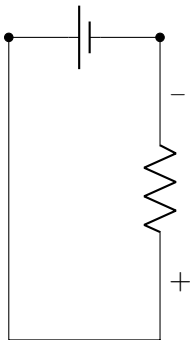


$$V = IR$$

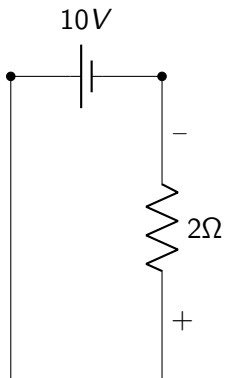


$$V = IR$$

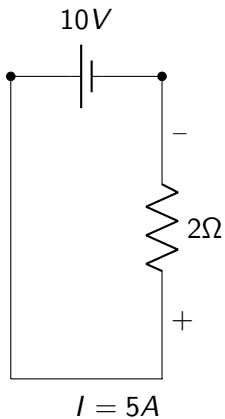


$$V = IR$$

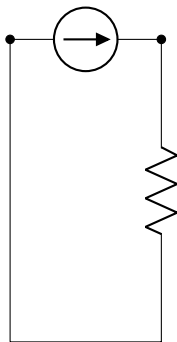

$$V = IR$$

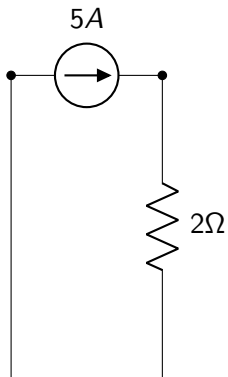


$$V = IR$$

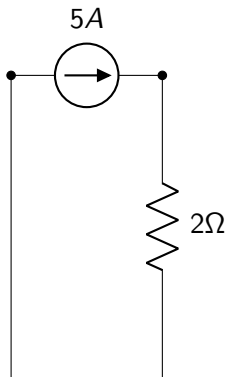

$$V = 10$$

(voltage drop of 10 Volts across resistor)


$$V = IR$$

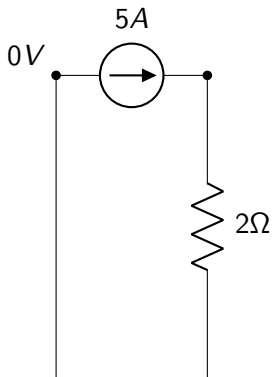

$$V = 10$$


(voltage drop of 10 Volts across resistor)

$$V = IR$$

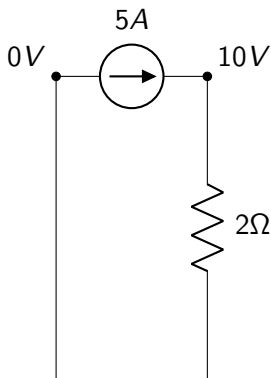

$$V = 10$$

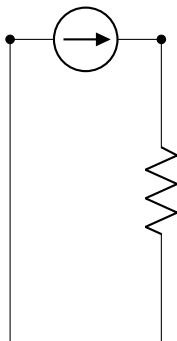(voltage drop of 10 Volts across resistor)





Find: currents through each resistor and each voltage source;
voltage drops across each current source


Find: currents through each resistor and each voltage source;
voltage drops across each current source


Kirchhoff's Laws

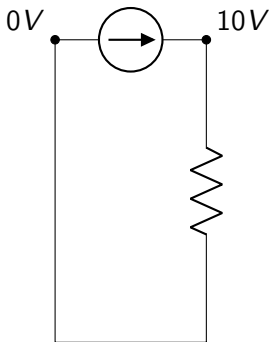1. The sum of voltage drops around any closed loops in the network must be zero.
2. For any node, current in equals current out




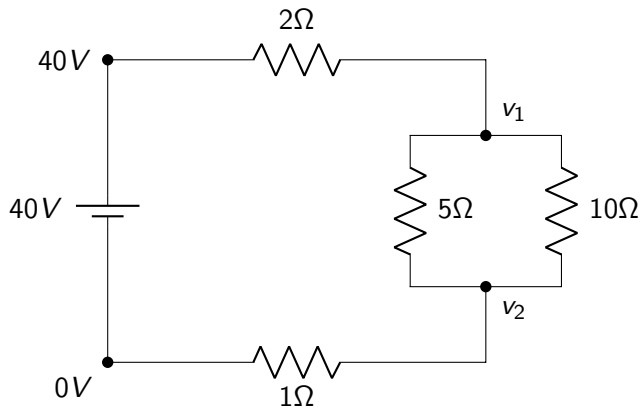

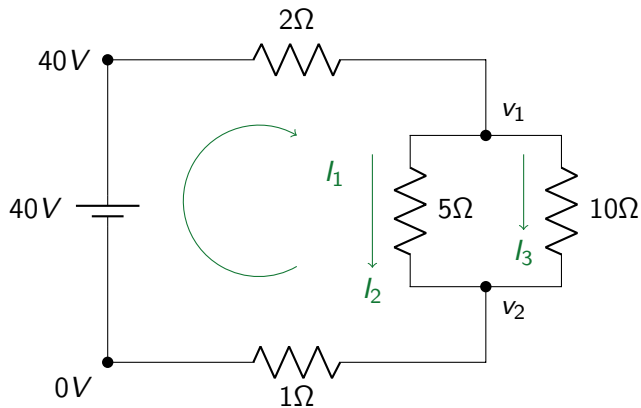


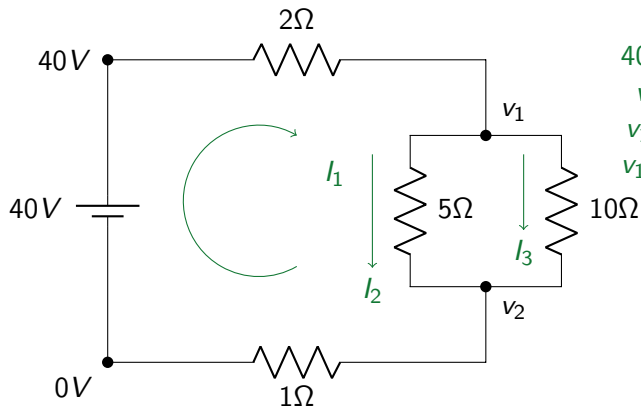

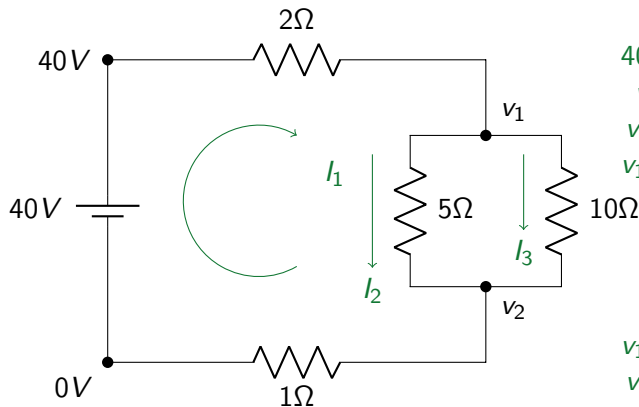
$$\begin{aligned} i_1 &= i_2 + i_3 \\ 40 - v_1 &= i_1 \cdot 2 \\ v_2 - 0 &= i_1 \cdot 1 \\ v_1 - v_2 &= 5i_2 \\ v_1 - v_2 &= 10i_3 \end{aligned}$$


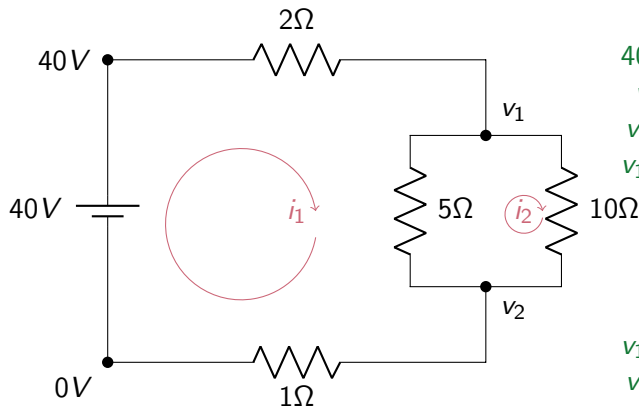
$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 40 - v_1 &= i_1 \cdot 2 \\
 v_2 - 0 &= i_1 \cdot 1 \\
 v_1 - v_2 &= 5i_2 \\
 v_1 - v_2 &= 10i_3 \\
 i_1 &= \frac{120}{19} \approx 6.3 \\
 i_2 &= \frac{80}{19} \approx 4.2 \\
 i_3 &= \frac{40}{19} \approx 2.1 \\
 v_1 &= \frac{520}{19} \approx 27.4 \\
 v_2 &= \frac{120}{19} \approx 6.3
 \end{aligned}$$



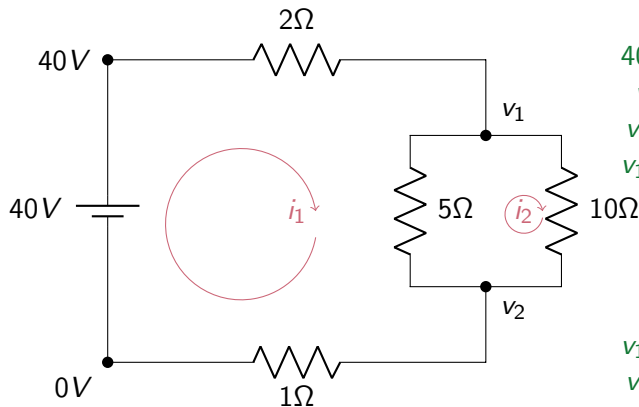
$$\begin{aligned} i_1 &= i_2 + i_3 \\ 40 - v_1 &= i_1 \cdot 2 \\ v_2 - 0 &= i_1 \cdot 1 \\ v_1 - v_2 &= 5i_2 \\ v_1 - v_2 &= 10i_3 \\ i_1 &= \frac{120}{19} \approx 6.3 \\ i_2 &= \frac{80}{19} \approx 4.2 \\ i_3 &= \frac{40}{19} \approx 2.1 \\ v_1 &= \frac{520}{19} \approx 27.4 \\ v_2 &= \frac{120}{19} \approx 6.3 \end{aligned}$$



$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 40 - v_1 &= i_1 \cdot 2 \\
 v_2 - 0 &= i_1 \cdot 1 \\
 v_1 - v_2 &= 5i_2 \\
 v_1 - v_2 &= 10i_3
 \end{aligned}$$

$$\begin{aligned}
 i_1 &= \frac{120}{19} \approx 6.3 \\
 i_2 &= \frac{80}{19} \approx 4.2 \\
 i_3 &= \frac{40}{19} \approx 2.1 \\
 v_1 &= \frac{520}{19} \approx 27.4 \\
 v_2 &= \frac{120}{19} \approx 6.3
 \end{aligned}$$
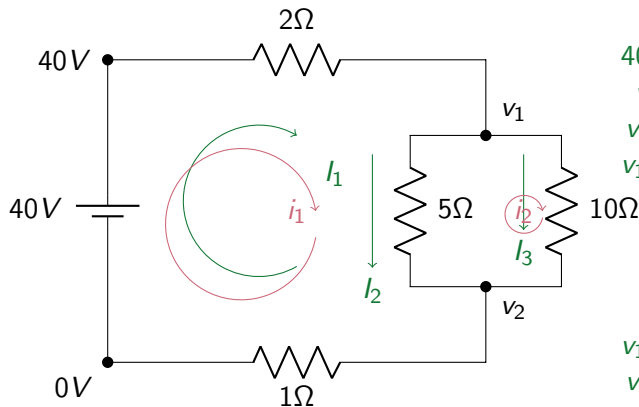
$$\begin{aligned}
 1i_1 - 40 + 2i_1 + 5(i_1 - i_2) &= 0 \\
 10i_2 + 5(i_2 - i_1) &= 0
 \end{aligned}$$



$$\begin{aligned} i_1 &= i_2 + i_3 \\ 40 - v_1 &= i_1 \cdot 2 \\ v_2 - 0 &= i_1 \cdot 1 \\ v_1 - v_2 &= 5i_2 \\ v_1 - v_2 &= 10i_3 \end{aligned}$$

$$\begin{aligned} i_1 &= \frac{120}{19} \approx 6.3 \\ i_2 &= \frac{80}{19} \approx 4.2 \\ i_3 &= \frac{40}{19} \approx 2.1 \\ v_1 &= \frac{520}{19} \approx 27.4 \\ v_2 &= \frac{120}{19} \approx 6.3 \end{aligned}$$

$$i_1 = \frac{120}{19}, i_2 = \frac{40}{19}$$

$$\begin{aligned} 1i_1 - 40 + 2i_1 + 5(i_1 - i_2) &= 0 \\ 10i_2 + 5(i_2 - i_1) &= 0 \end{aligned}$$

Things to Keep in Mind


- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.

Things to Keep in Mind

- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current


Things to Keep in Mind

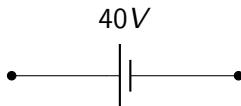- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.




Things to Keep in Mind

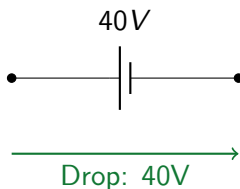- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.



Things to Keep in Mind

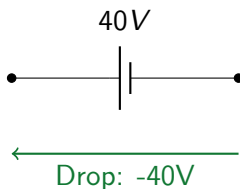- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.




Things to Keep in Mind

- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




Things to Keep in Mind

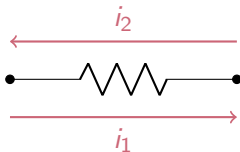- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




Things to Keep in Mind

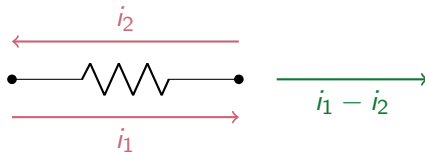
- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.





Things to Keep in Mind

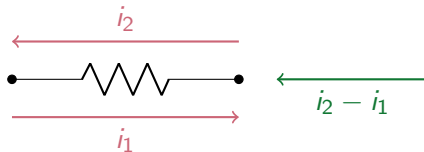- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.



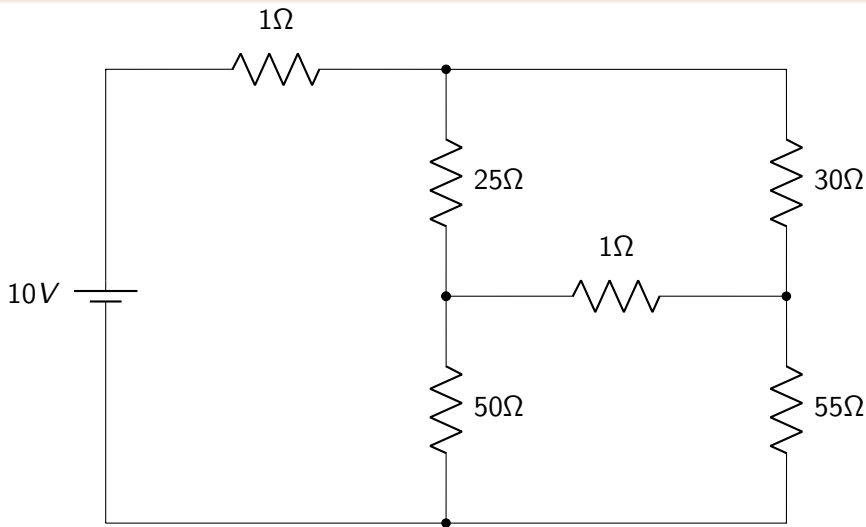

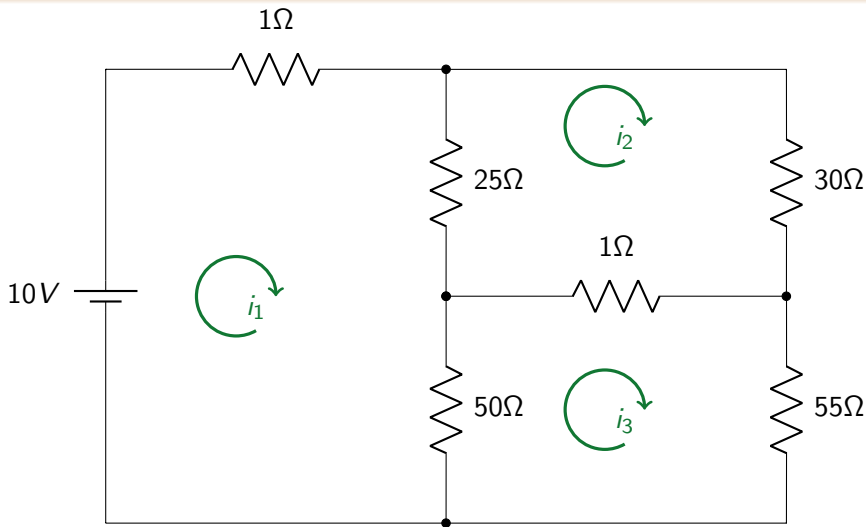

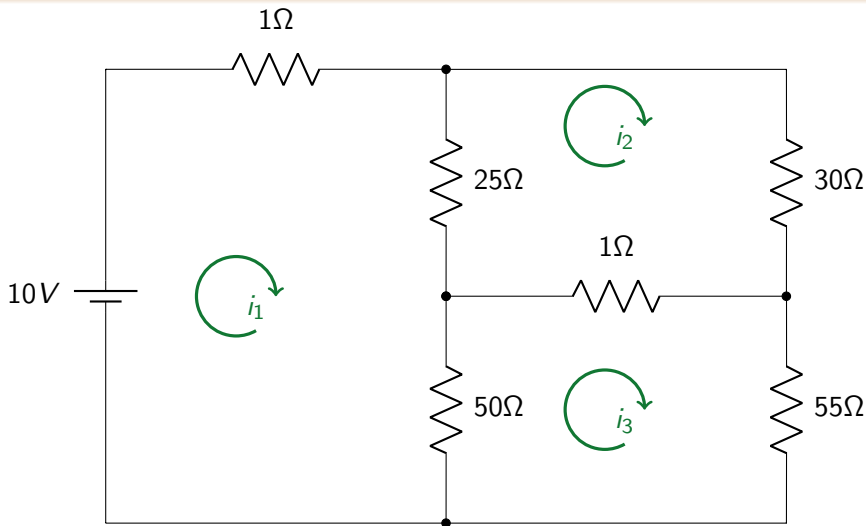

$$i_1 \approx 0.2449, \quad i_2 \approx 0.1114, \quad i_3 \approx 0.1166$$

Equations from previous slide:

$$i_1 \text{ loop: } -10 + i_1 + 25(i_1 - i_2) + 50(i_1 - i_3) = 0$$

$$i_2 \text{ loop: } 25(i_2 - i_1) + 30i_2 + (i_2 - i_3) = 0$$

$$i_3 \text{ loop: } 50(i_3 - i_1) + (i_3 - i_2) + 55i_3 = 0$$

$$76i_1 - 25i_2 - 50i_3 = 10$$

$$-25i_1 + 56i_2 - i_3 = 0$$

$$-50i_1 - i_2 + 106i_3 = 0$$

Things to Keep in Mind


- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.

Things to Keep in Mind

- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current


Things to Keep in Mind

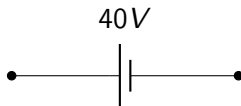- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.




Things to Keep in Mind

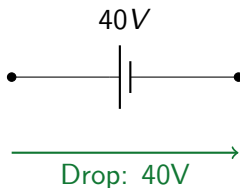- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.



Things to Keep in Mind

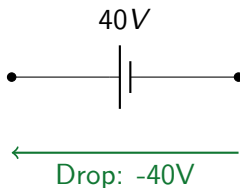- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.




Things to Keep in Mind

- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




Things to Keep in Mind

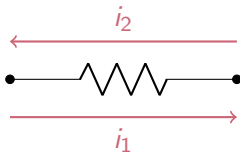- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




Things to Keep in Mind

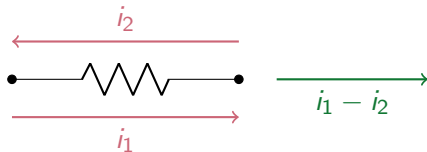
- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.





Things to Keep in Mind

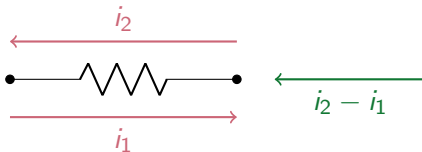- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.



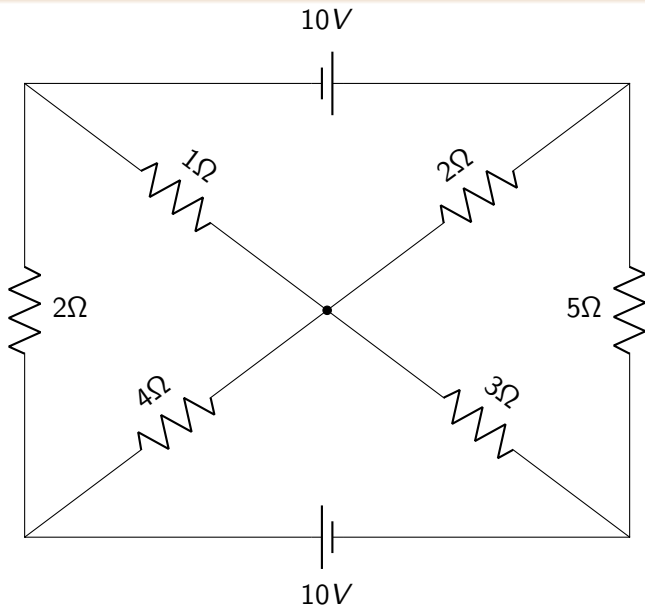

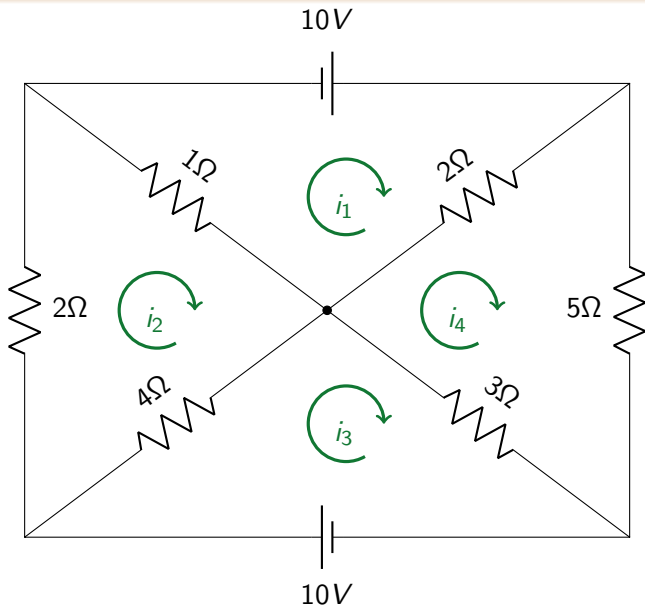

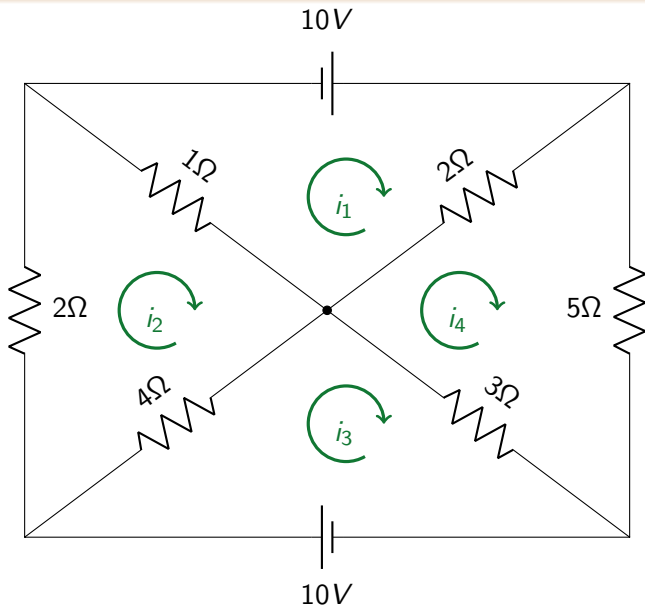

$$i_1 \approx 6.2321 \quad i_2 \approx 3.4821 \quad i_3 \approx 4.5357 \quad i_4 \approx 2.6071$$

Equations from Previous Slide:

$$i_1 \text{ loop: } -10 + 2(i_1 - i_4) + (i_1 - i_2) = 0$$

$$i_2 \text{ loop: } 2i_2 + (i_2 - i_1) + 4(i_2 - i_3) = 0$$

$$i_3 \text{ loop: } -10 + 4(i_3 - i_2) + 3(i_3 - i_4) = 0$$

$$i_4 \text{ loop: } 5i_4 + 3(i_4 - i_3) + 2(i_4 - i_1) = 0$$

$$\begin{array}{rcccccccl} 3i_1 & - & i_2 & + & 0i_3 & - & 2i_4 & = & 10 \\ -i_1 & + & 7i_2 & - & 4i_3 & + & 0i_4 & = & 0 \\ 0i_1 & - & 4i_2 & + & 7i_3 & - & 3i_4 & = & 10 \\ -2i_1 & + & 0i_2 & - & 3i_3 & + & 10i_4 & = & 0 \end{array}$$

Things to Keep in Mind


- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.

Things to Keep in Mind

- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current


Things to Keep in Mind

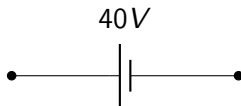- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.




Things to Keep in Mind

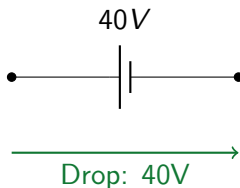- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.



Things to Keep in Mind

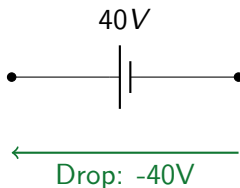- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.




Things to Keep in Mind

- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




Things to Keep in Mind

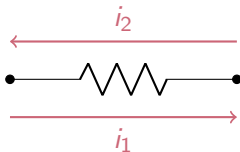- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




Things to Keep in Mind

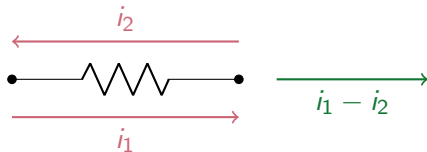
- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.



Things to Keep in Mind

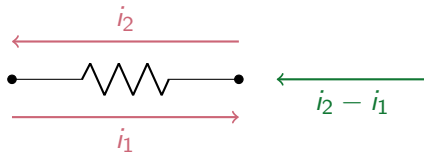
- Set up your loop currents in any direction (clockwise or counter-clockwise), then follow them around in that direction.
- If your actual flow is not in the direction you chose, you'll simply get a negative number for your current
- We're counting up voltage drops around a loop. A voltage DROP is high to low.
- Branch current is the NET effect of the loop currents.




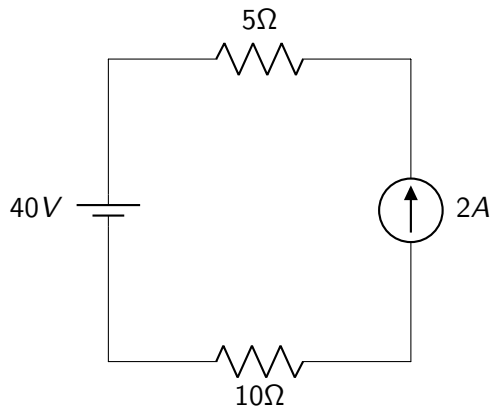



$$V = IR = \overset{\leftarrow}{2} \times 5 = 10$$


5Ω

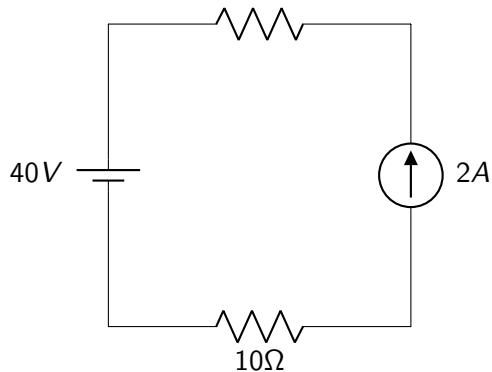


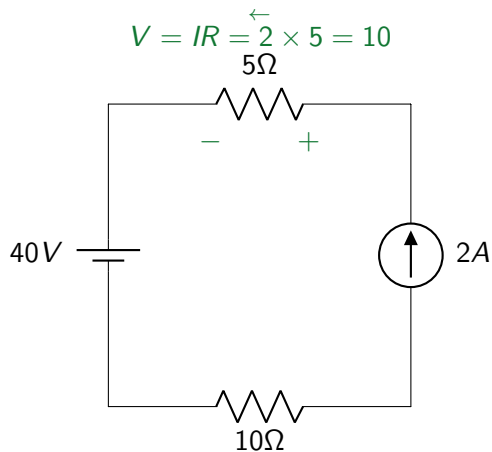


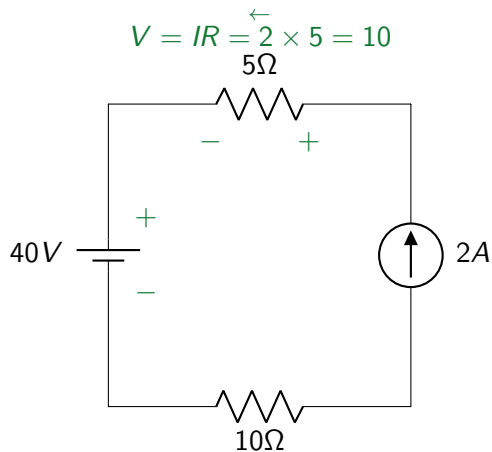


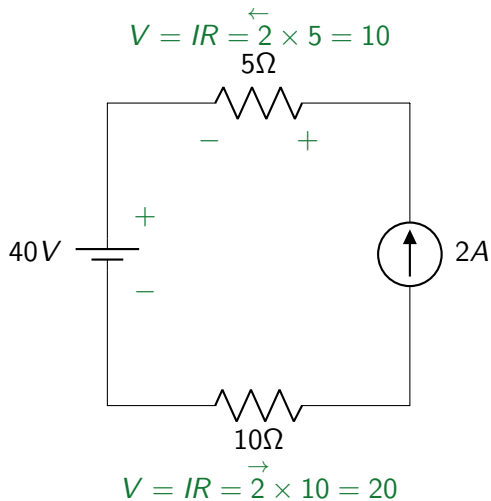


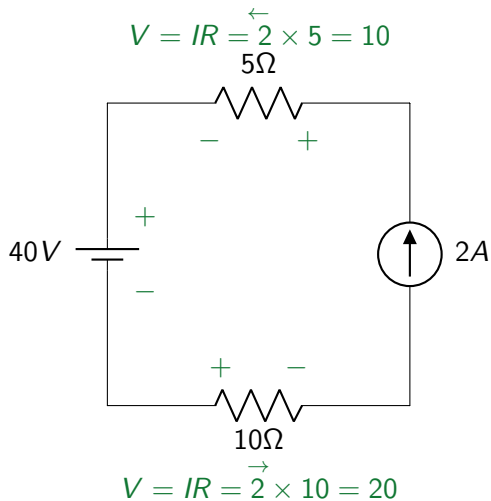


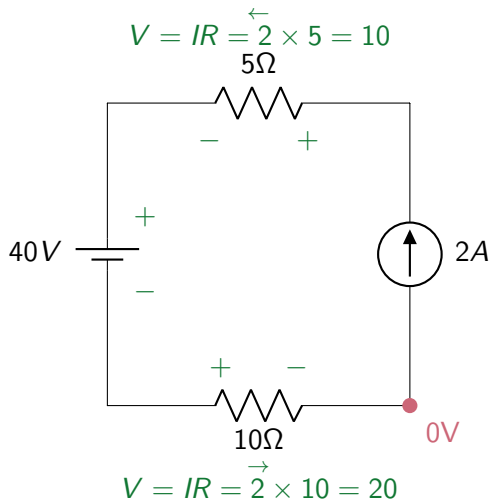

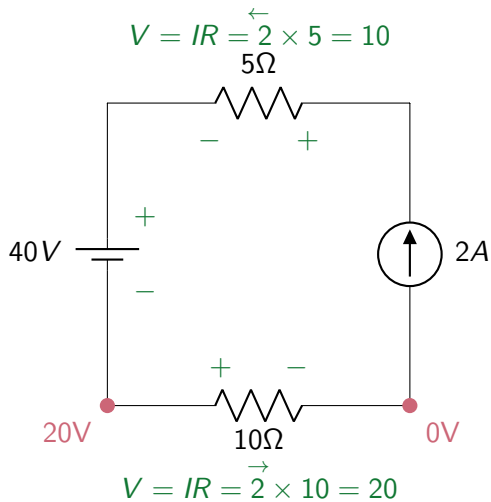


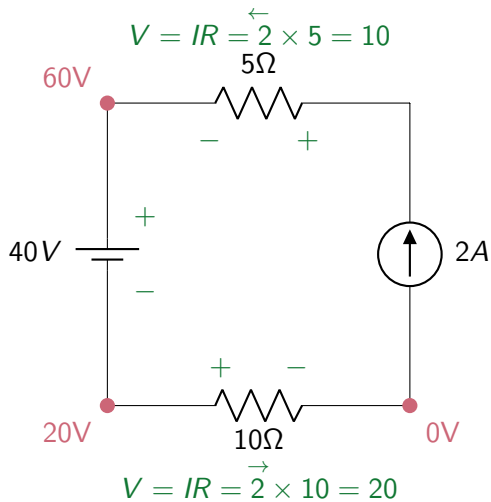


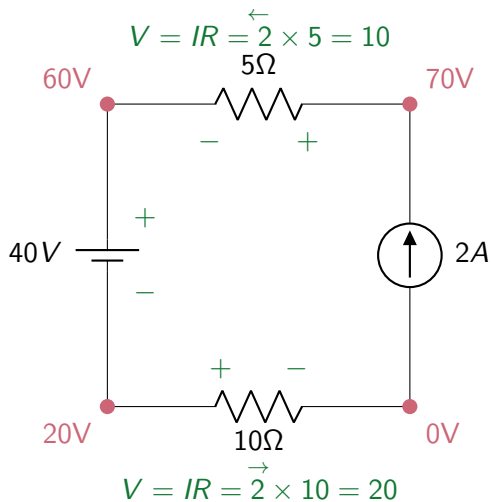


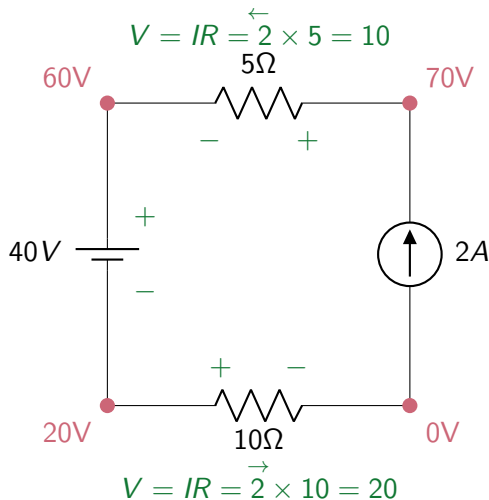

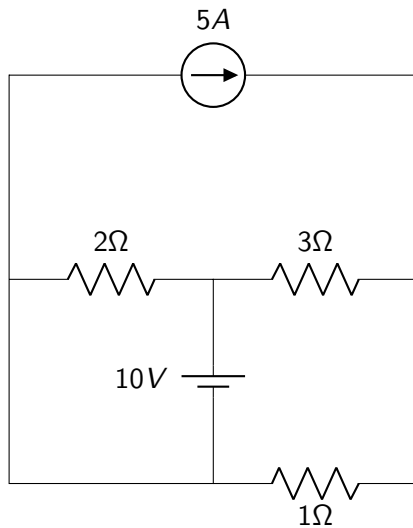
We can imagine replacing the current source with a 70V voltage source, which overpowers the 40V source.




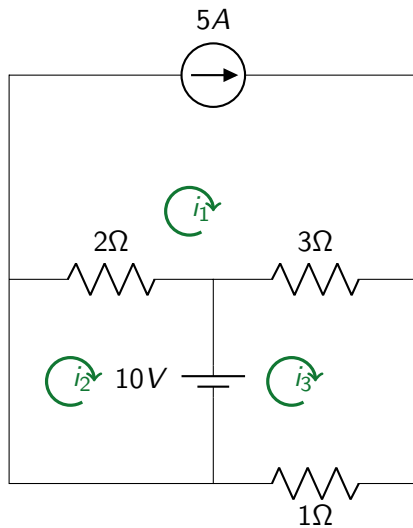


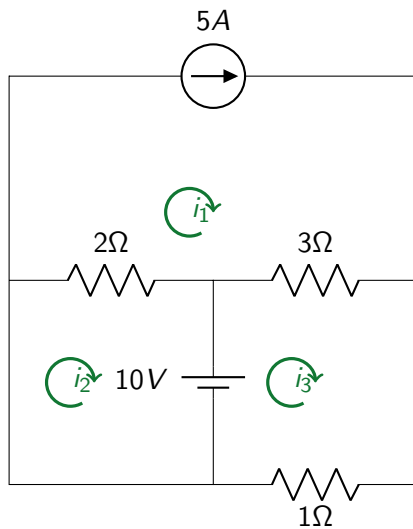

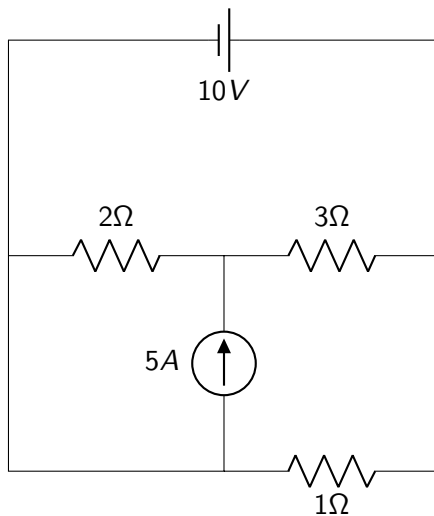
$$i_1 = 5, \quad i_2 = 0, \quad i_3 = \frac{25}{4}$$



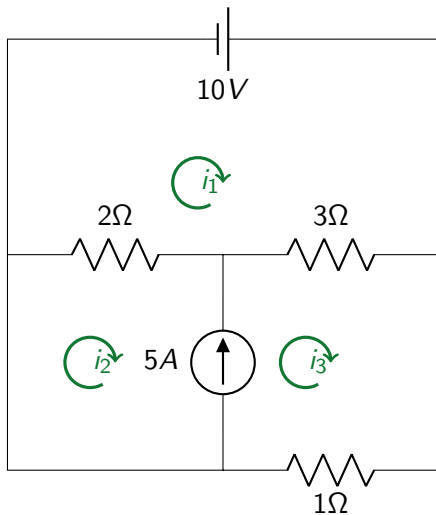

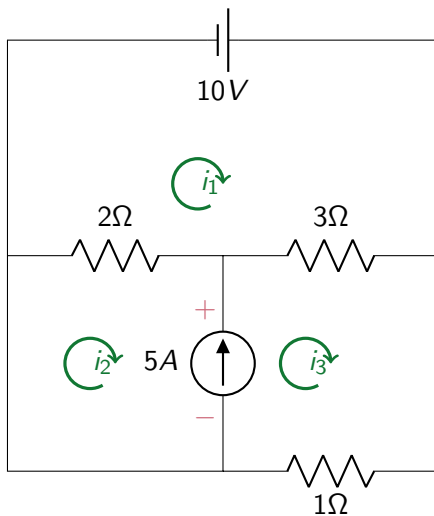

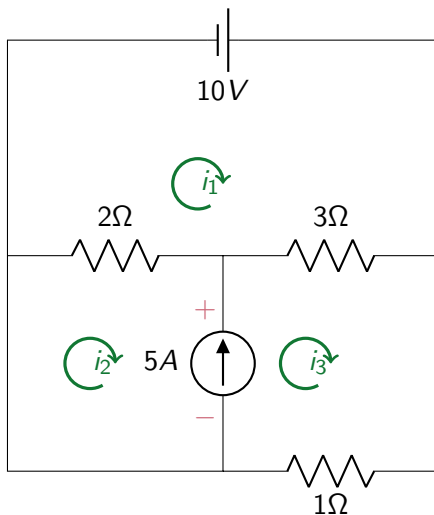Let E be the voltage drop across the current source.



Let E be the voltage drop across the current source.

$$i_1 = 10, \quad i_2 = 5, \quad i_3 = 10, \quad E = 10$$

Equations from previous slide:


Current Source: $5 = i_3 - i_2$


i_1 **Loop:** $-10 + 3(i_1 - i_3) + 2(i_1 - i_2) = 0$


i_2 **Loop:** $2(i_2 - i_1) + E = 0$


i_3 **Loop:** $-E + 3(i_3 - i_1) + i_3 = 0$
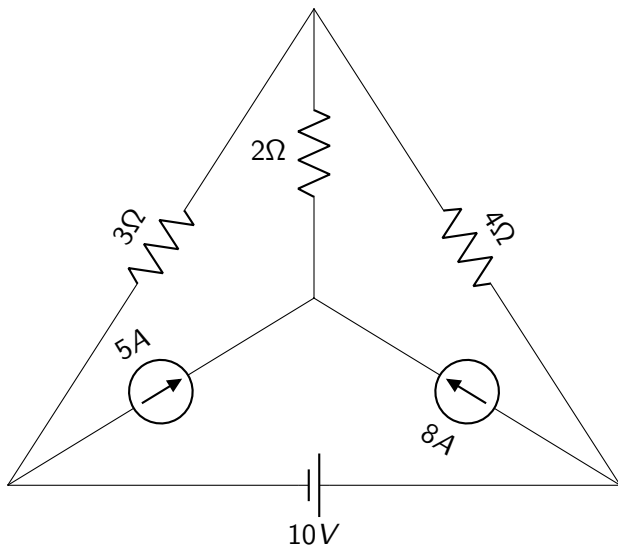
$$\begin{array}{rcccccccl} 0i_1 & - & i_2 & + & i_3 & + & 0E & = & 5 \\ 5i_1 & - & 2i_2 & - & 3i_3 & + & 0E & = & 10 \\ -2i_1 & + & 2i_2 & + & 0i_3 & + & E & = & 0 \\ -3i_1 & + & 0i_2 & + & 4i_3 & - & E & = & 0 \end{array}$$



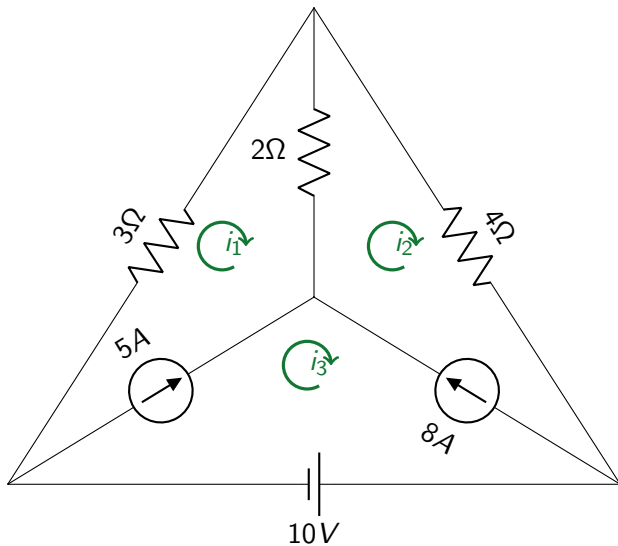

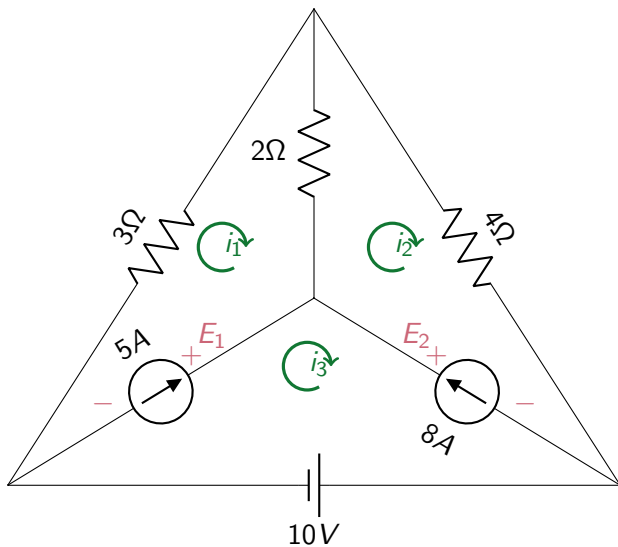

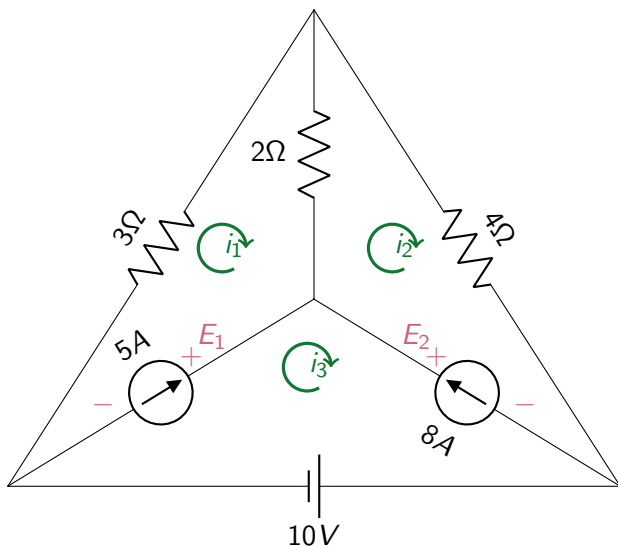

$$i_1 \approx -8.8571,$$

$$i_2 \approx 4.1429,$$

$$i_3 \approx -3.8571,$$

$$E_1 \approx 52.5714,$$

$$E_2 \approx 42.5714$$

Equations from previous slide:

5A Current Source: $i_3 - i_1 = 5$


8A Current Source: $i_2 - i_3 = 8$


i_1 Loop: $3i_1 + 2(i_1 - i_2) + E_1 = 0$


i_2 Loop: $2(i_2 - i_1) + 4i_2 - E_2 = 0$

i_3 Loop: $-E_1 + E_2 + 10 = 0$

$-i_1$	+	$0i_2$	+	i_3	+	$0E_1$	+	$0E_2$	=	5
$0i_1$	+	i_2	-	i_3	+	$0E_1$	+	$0E_2$	=	8
$5i_1$	-	$2i_2$	+	$0i_3$	+	E_1	+	$0E_2$	=	0
$-2i_1$	+	$6i_2$	+	$0i_3$	+	$0E_1$	-	E_2	=	0
$0i_1$	+	$0i_2$	+	$0i_3$	-	E_1	+	E_2	=	-10

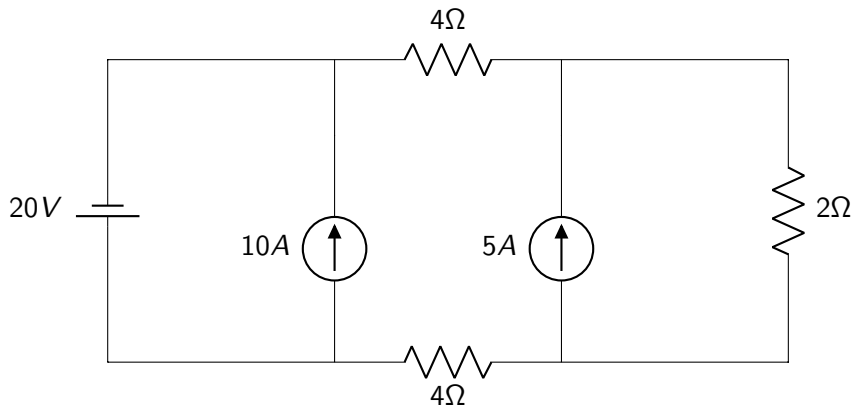

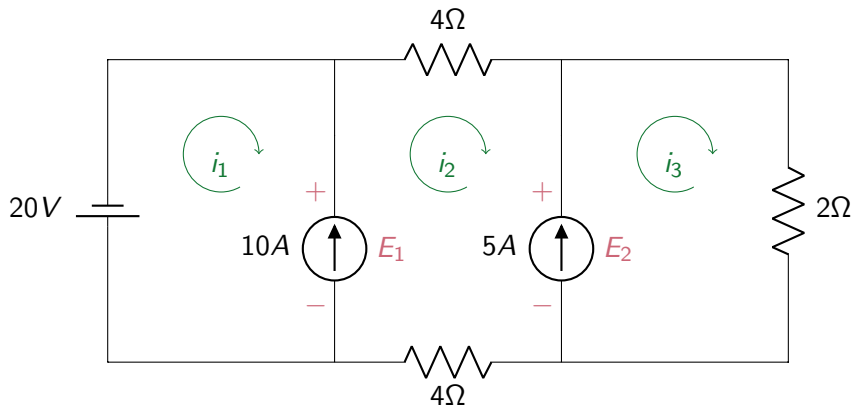

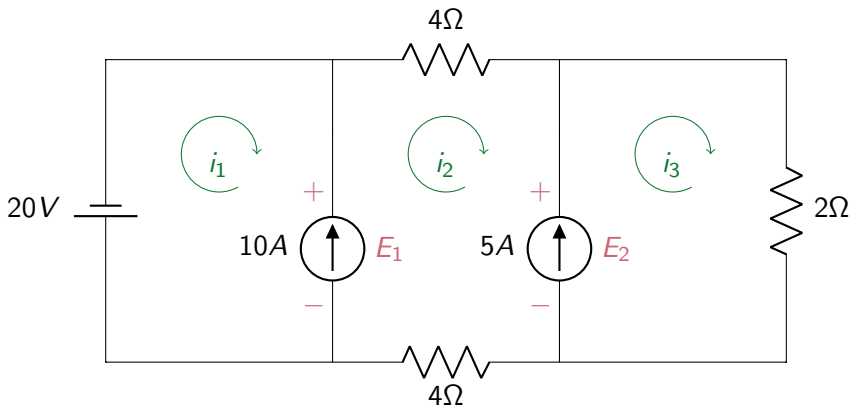

$$i_1 = -13A, \quad i_2 = -3A, \quad i_3 = 2A, \quad E_1 = -20V, \quad E_2 = 4V$$

Current across voltage source: 13A, top to bottom

Equations from previous slide:

10A Current Source: $i_2 - i_1 = 10$


5A Current Source: $i_3 - i_2 = 5$


i_1 Loop: $20 + E_1 = 0$

i_2 Loop: $4i_2 + E_2 + 4i_2 - E_1 = 0$


i_3 Loop: $2i_3 - E_2 = 0$
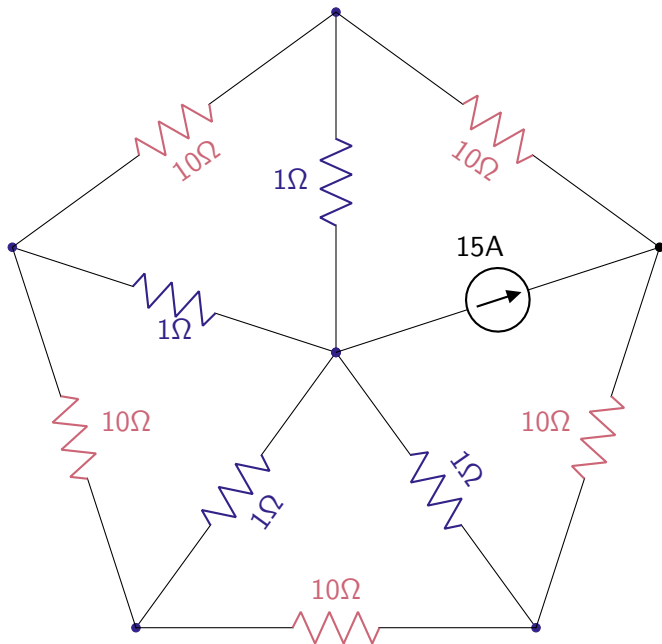
$$\begin{array}{rclclclclclcl}
 -i_1 & + & i_2 & + & 0i_3 & + & 0E_1 & + & 0E_2 & = & 10 \\
 0i_1 & - & i_2 & + & i_3 & + & 0E_1 & + & 0E_2 & = & 5 \\
 0i_1 & + & 0i_2 & + & 0i_3 & + & E_1 & + & 0E_2 & = & -20 \\
 0i_1 & + & 8i_2 & + & 0i_3 & - & E_1 & + & E_2 & = & 0 \\
 0i_1 & + & 0i_2 & + & 2i_3 & + & 0E_1 & - & E_2 & = & 0
 \end{array}$$




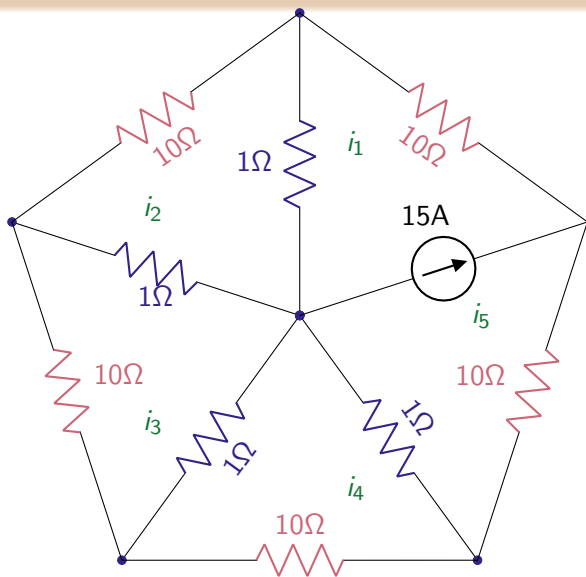

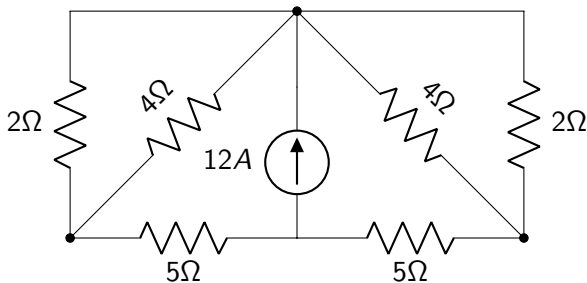
clockwise: $i_1 = -7.5$, $i_2 = -1/12$, $i_3 = 0$, $i_4 = 1/12$, $i_5 = 7.5$




Find all branch currents.

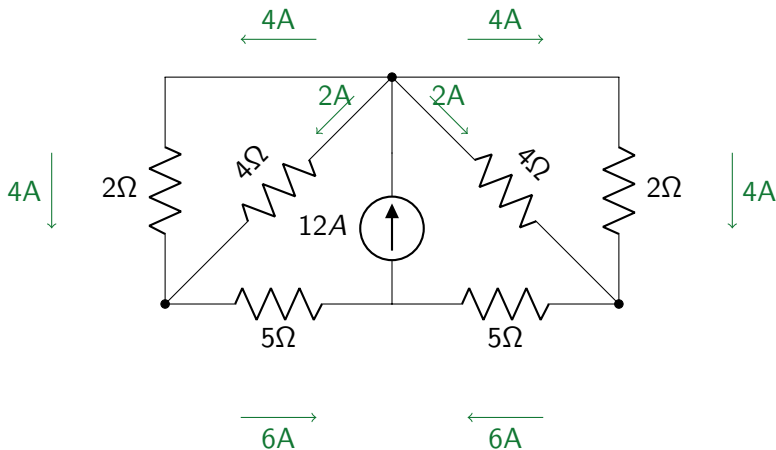


Find all branch currents.

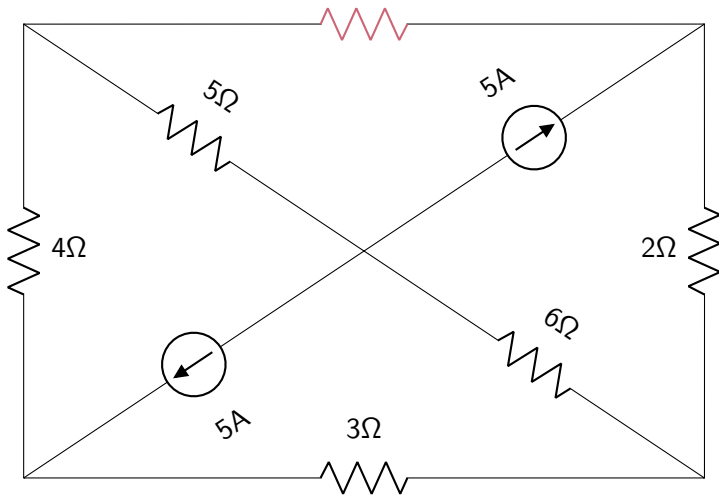

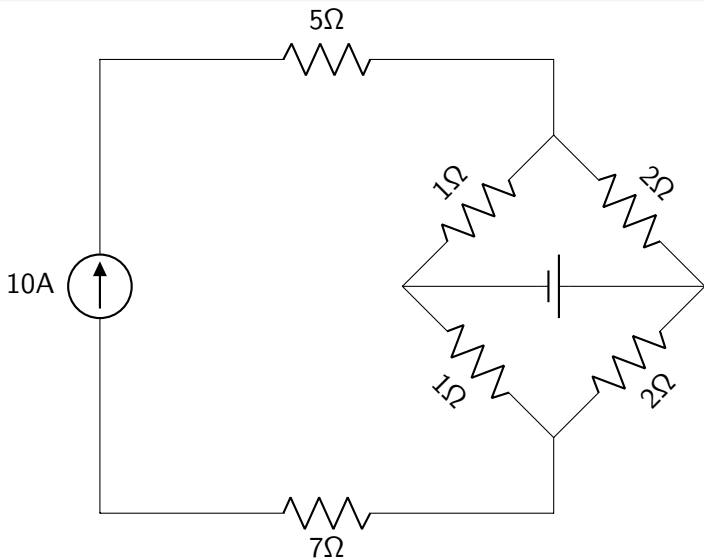What resistance should the top resistor have, if you want each wire touching the centre to have current 5A ?



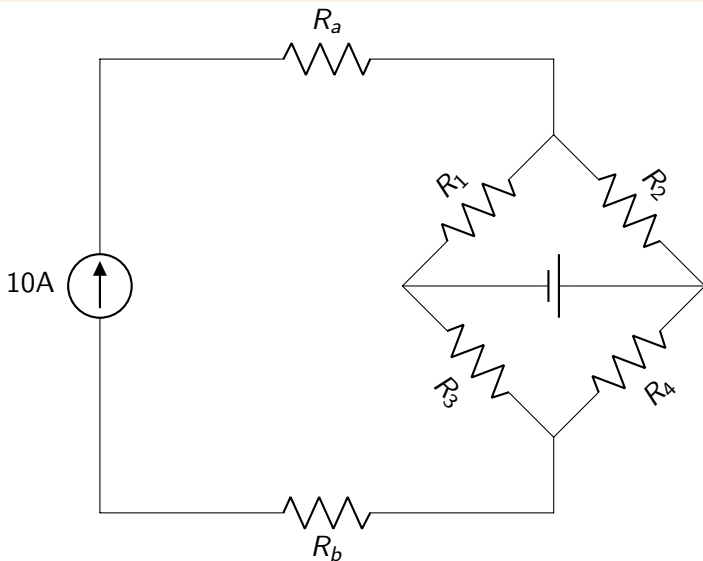What voltage should the voltage source have, in order for there to be no current across it?



What voltage should the voltage source have, in order for there to be no current across it?