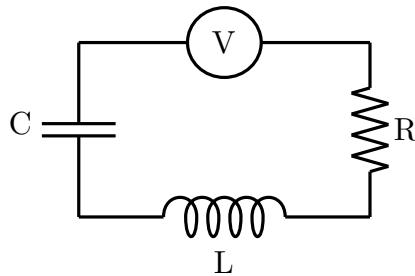


# The RLC Circuit

The RLC circuit is the electrical circuit consisting of a resistor of resistance  $R$ , a coil of inductance  $L$ , a capacitor of capacitance  $C$  and a voltage source arranged in series.



If the charge on the capacitor is  $Q$  and the current flowing in the circuit is  $I$ , the voltage across  $R$ ,  $L$  and  $C$  are  $RI$ ,  $L\frac{dI}{dt}$  and  $\frac{Q}{C}$  respectively. By the Kirchhoff's law that says that the voltage between any two points has to be independent of the path used to travel between the two points,

$$LI'(t) + RI(t) + \frac{1}{C}Q(t) = V(t)$$

Assuming that  $R$ ,  $L$ ,  $C$  and  $V$  are known, this is still one differential equation in two unknowns,  $I$  and  $Q$ . However the two unknowns are related by  $I(t) = \frac{dQ}{dt}(t)$  so that

$$LQ''(t) + RQ'(t) + \frac{1}{C}Q(t) = V(t)$$

or, differentiating with respect to  $t$  before subbing in  $\frac{dQ}{dt}(t) = I(t)$ ,

$$LI''(t) + RI'(t) + \frac{1}{C}I(t) = V'(t)$$

For an ac voltage source, choosing the origin of time so that  $V(0) = 0$ ,  $V(t) = E_0 \sin(\omega t)$  and the differential equation becomes

$$LI''(t) + RI'(t) + \frac{1}{C}I(t) = \omega E_0 \cos(\omega t) \tag{1}$$

## The General Solution

Let us look for a particular solution of (1) of the form  $I(t) = A \sin(\omega t - \varphi)$  with the amplitude  $A$  and phase  $\varphi$  to be determined. Any such particular solution must obey

$$\begin{aligned} -L\omega^2 A \sin(\omega t - \varphi) + R\omega A \cos(\omega t - \varphi) + \frac{1}{C} A \sin(\omega t - \varphi) &= \omega E_0 \cos(\omega t) \\ &= \omega E_0 \cos(\omega t - \varphi + \varphi) \end{aligned}$$

and hence

$$\left(\frac{1}{C} - L\omega^2\right) A \sin(\omega t - \varphi) + R\omega A \cos(\omega t - \varphi) = \omega E_0 \cos(\varphi) \cos(\omega t - \varphi) - \omega E_0 \sin(\varphi) \sin(\omega t - \varphi)$$

Matching coefficients of  $\sin(\omega t - \varphi)$  and  $\cos(\omega t - \varphi)$  on the left and right hand sides gives

$$(L\omega^2 - \frac{1}{C})A = \omega E_0 \sin(\varphi) \tag{2}$$

$$R\omega A = \omega E_0 \cos(\varphi) \tag{3}$$

It is now easy to solve for  $A$  and  $\varphi$

$$\begin{aligned} \frac{(2)}{(3)} &\implies \tan(\varphi) = \frac{L\omega^2 - \frac{1}{C}}{R\omega} && \implies \varphi = \tan^{-1}\left(\frac{L\omega}{R} - \frac{1}{RC\omega}\right) \\ \sqrt{(2)^2 + (3)^2} &\implies \sqrt{(L\omega^2 - \frac{1}{C})^2 + R^2\omega^2} A = \omega E_0 && \implies A = \frac{\omega E_0}{\sqrt{(L\omega^2 - \frac{1}{C})^2 + R^2\omega^2}} \end{aligned} \tag{4}$$

Assuming that  $R^2 \neq 4L/C$ , the complementary solution for (1) is

$$c_1 e^{r_1 t} + c_2 e^{r_2 t}$$

where

$$r_{1,2} = \frac{-R \pm \sqrt{R^2 - 4L/C}}{2L} \tag{5}$$

are the two roots of

$$Lr^2 + Rr + \frac{1}{C} = 0$$

Hence, the general solution of (1) is

$$I(t) = c_1 e^{r_1 t} + c_2 e^{r_2 t} + A \sin(\omega t - \varphi)$$

with  $r_1$ ,  $r_2$  given in (5) and  $A$ ,  $\varphi$  given in (4). The arbitrary constants  $c_1$  and  $c_2$  are determined by initial conditions. However, when  $e^{r_1 t}$  and  $e^{r_2 t}$  damp out quickly, as is often the case, their values don't matter.