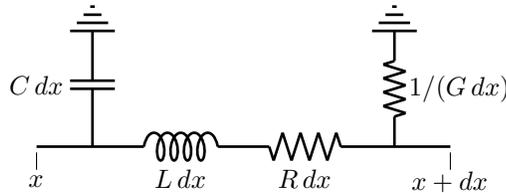


## Derivation of the Telegraph Equation

Model an infinitesimal piece of telegraph wire as an electrical circuit which consists of a resistor of resistance  $R dx$  and a coil of inductance  $L dx$ . If  $i(x, t)$  is the current through the wire, the voltage across the resistor is  $iR dx$  while that across the coil is  $\frac{\partial i}{\partial t} L dx$ . Denoting by  $u(x, t)$  the voltage at position  $x$  and time  $t$ , we have that the change in voltage between the ends of the piece of wire is

$$du = -iR dx - \frac{\partial i}{\partial t} L dx$$

Suppose further that current can escape from the wire to ground, either through a resistor of conductance  $G dx$  or through a capacitor of capacitance  $C dx$ . The amount that escapes through the resistor is  $uG dx$ .



Because the charge on the capacitor is  $q = uC dx$ , the amount of current that escapes through the capacitor is  $q_t = u_t C dx$ . In total

$$di = -uG dx - u_t C dx$$

Dividing by  $dx$  and taking the limit  $dx \searrow 0$  we get the differential equations

$$u_x + Ri + Li_t = 0 \tag{1}$$

$$Cu_t + Gu + i_x = 0 \tag{2}$$

Solving (2) for  $i_x$  gives  $i_x = -Cu_t - Gu$ . Substituting this and its consequence  $i_{xt} = -Cu_{tt} - Gu_t$  into  $\frac{\partial}{\partial x}(1)$ , which is  $u_{xx} + Ri_x + Li_{xt} = 0$ , gives

$$u_{xx} + R(-Cu_t - Gu) + L(-Cu_{tt} - Gu_t) = 0$$

Dividing by  $LC$  and moving some terms to the other side of the equation gives

$$\frac{1}{LC}u_{xx} = u_{tt} + \left(\frac{R}{L} + \frac{G}{C}\right)u_t + \frac{GR}{LC}u$$

Renaming some constants, we get the *telegraph equation*

$$u_{tt} + (\alpha + \beta)u_t + \alpha\beta u = c^2 u_{xx}$$

where

$$c^2 = \frac{1}{LC} \quad \alpha = \frac{G}{C} \quad \beta = \frac{R}{L}$$