

Using new notation:

$$Dv = \begin{bmatrix} j_1 R_1 \\ j_2 R_2 \\ \vdots \\ j_5 R_5 \end{bmatrix} = \underbrace{\begin{bmatrix} R_1 & & 0 \\ & R_2 & \\ 0 & & \ddots \\ & & & R_5 \end{bmatrix}}_R \underbrace{\begin{bmatrix} j_1 \\ j_2 \\ \vdots \\ j_5 \end{bmatrix}}_{\vec{j}}$$

$\uparrow$   
(matrix)

So,

$$Dv = R\vec{j} \Rightarrow R^{-1}Dv = \vec{j}$$

where  $R^{-1} = \begin{bmatrix} 1/R_1 & & 0 \\ & \ddots & \\ 0 & & 1/R_5 \end{bmatrix}$ .

Next, let's calculate

① ⑤

the current accumulating at each vertex:

$$\vec{z} = D^T \vec{j} = \underbrace{D^T R^{-1} D}_{\text{matrix}} v$$

$$\begin{bmatrix} z_1 \\ z_2 \\ z_3 \\ z_4 \end{bmatrix} \left\{ \begin{array}{l} \text{current} \\ \text{accumulating} \\ \text{at vertex } i. \end{array} \right.$$

Definition: The matrix

$$L = D^T R^{-1} D$$

is called the Laplacian of the circuit.

Remark:  $L$  is symmetric:  $L^T = L$ .

Pf:  $(D^T R^{-1} D)^T = D^T (R^{-1})^T (D^T)^T$   
 $L^T = D^T R^{-1} D = L$

Ex: Let's calculate the Laplacian of the circuit above, with

$$R_1 = R_2 = \dots = R_5 = 1.$$

$$L = D^T \cdot I \cdot D = D^T D = \begin{bmatrix} 2 & -1 & 0 & -1 \\ -1 & 3 & -1 & -1 \\ 0 & -1 & 2 & -1 \\ -1 & -1 & -1 & 3 \end{bmatrix}$$

Note: If all the resistors are  $1\Omega$ , then  $L$  is such that:

$L_{ii} = \#$  of neighbours of vertex  $i$

$$L_{ij} = \begin{cases} -1 & \text{if vertex } i \text{ \& } j \text{ are connected} \\ 0 & \text{if " " not connected} \end{cases}$$

What if  $R_j \neq 1$ ?

$$L_{ii} = \sum_j \frac{1}{R_j}, \text{ sum over all edges connecting to vertex } i$$

$$L_{ij} = \begin{cases} -\frac{1}{R_k} & \text{if } i \text{ --- } R_k \text{ --- } j \\ 0 & \text{otherwise} \end{cases}$$

Back to currents:

$$\vec{z} = D^T R^{-1} D v = L v$$

(current accumulating @ each node)

Kirchoff's law:

$$L \vec{v} = \vec{0}$$

(no current accumulates at any node (unless there are power sources involved)).

An immediate implication:

For a connected circuit with no power source,

$$L \vec{v} = 0 \Leftrightarrow D^T R^{-1} D v = \vec{0}$$

$$\Leftrightarrow D v = 0 \Leftrightarrow v = c \cdot \begin{bmatrix} 1 \\ \vdots \\ 1 \end{bmatrix}$$

↑ needs proof \*

(2)



In other words, in a connected circuit with no power source, all nodes are at the same voltage level, and no current is flowing through the circuit.

Prop.  $N(L) = N(D)$ .

- Let  $x \in N(D)$ . Then  $Dx = \vec{0}$   
 $\Rightarrow Lx = D^T R^{-1} (Dx) = D^T R^{-1} \vec{0} = \vec{0}$   
 $\Rightarrow x \in N(L)$ . Then  $N(D) \subseteq N(L)$ .

Let  $y \in N(L)$ . Then

$$Ly = D^T R^{-1} D y = \vec{0}$$

$$\Rightarrow y^T L y = \underbrace{y^T D^T}_{w^T} R^{-1} \underbrace{D y}_w = 0.$$

$$\Rightarrow w^T R^{-1} w = 0$$

$$\Leftrightarrow [w_1 \ w_2 \ \dots \ w_n] \begin{bmatrix} 1/R_1 & & 0 \\ & \ddots & \\ 0 & & 1/R_n \end{bmatrix} \begin{bmatrix} w_1 \\ \vdots \\ w_n \end{bmatrix} = 0 \quad (3)$$

$$\Leftrightarrow [w_1 \ w_2 \ \dots \ w_n] \begin{bmatrix} 1/R_1 w_1 \\ \vdots \\ 1/R_n w_n \end{bmatrix} = 0.$$

$$\Leftrightarrow \frac{1}{R_1} w_1^2 + \frac{1}{R_2} w_2^2 + \dots + \frac{1}{R_n} w_n^2 = 0$$


Since  $\frac{1}{R_j} > 0$  and  $w_j^2 \geq 0$

$$\Leftrightarrow w_1 = w_2 = \dots = w_n = 0.$$

$$\Leftrightarrow Dy = \vec{0} \quad (\text{remember } w = Dy)$$

$$\Rightarrow y \in N(D).$$

## Connecting a battery:

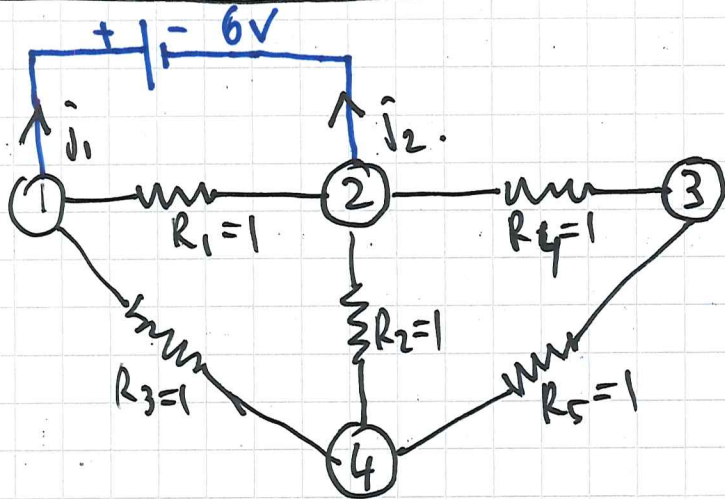

What changes:

~~$v_1 = 6$ ;  $v_2 = 0$~~

- $v_1 = b_1$ ;  $v_2 = b_2$

(in our example:  $v_1 = 6$ ;  $v_2 = 0$ ).

- $\hat{j}_1$  and  $\hat{j}_2$  are currents such that

$$\hat{j}_1 = -\hat{j}_2.$$

Let's compute the currents accumulating at each vertex:

$$L v = z$$

Where:

$$\begin{bmatrix} 2 & -1 & 0 & -1 \\ -1 & 3 & -1 & -1 \\ 0 & -1 & 2 & -1 \\ -1 & -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} v_1 = b_1 \\ v_2 = b_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} j_1 \\ j_2 \\ 0 \\ 0 \end{bmatrix}$$

Above:  $b_1, b_2$  fixed (known)

$v_3, v_4, j_1, j_2$  unknown

This system is of the form

$$\begin{bmatrix} A & B^T \\ B & C \end{bmatrix} \begin{bmatrix} \vec{b} \\ \vec{v} \end{bmatrix} = \begin{bmatrix} \vec{j} \\ \vec{0} \end{bmatrix}$$

*unknowns*

where  $A = \begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}$ ,  $B = \begin{bmatrix} 0 & -1 \\ -1 & -1 \end{bmatrix}$ ,

Then:

$$\begin{cases} A b + B^T v = j & (1) \\ B b + C v = 0 & (2) \end{cases}$$





From (2):  $-Bb = Cv$

$$\Rightarrow \boxed{v = -C^{-1}Bb}$$

↳ plug into (1):

$$Ab - B^T C^{-1} B b = J$$

$$\Rightarrow \underbrace{(A - B^T C^{-1} B)}_M b = J$$


$M$  ← known quantity

Ex: In our example,

$$M = \frac{8}{5} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}; \quad b = \begin{bmatrix} 6 \\ 0 \end{bmatrix};$$

$$J = \frac{8}{5} \begin{bmatrix} 6 \\ -6 \end{bmatrix}.$$

How to interpret?

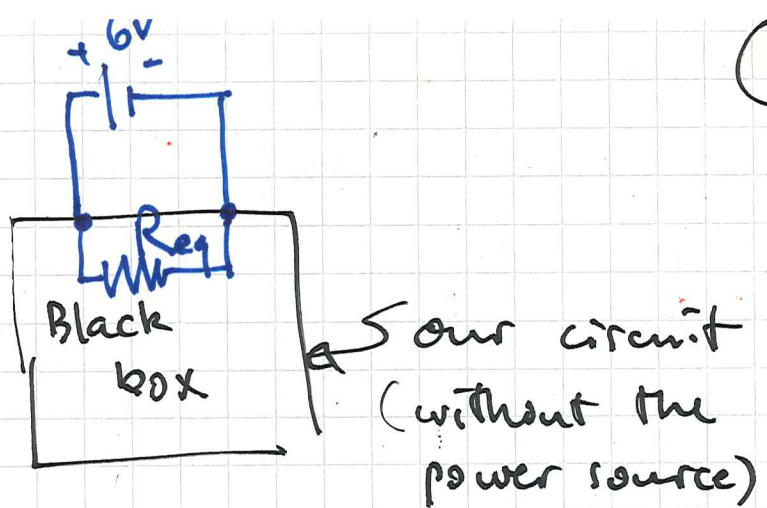

$R_{eq}$ : equivalent resistance for the whole black box.

Current:  $\frac{8}{5} \times 6$ .

voltage: 6

$$\Rightarrow R_{eq} = \frac{6}{\frac{8}{5} \times 6} = \frac{1}{\frac{8}{5}} = \frac{5}{8}.$$

↑  
equivalent resistance of the network.